

This wiring demonstrates how to wire the motor drivers so that the enable pins are independently driven by Arduino pins 8-11.

Also shows how the teensy is wired up as a usbHost

